 


# EECS 281: Homework #1 Problem 1 (1a SPICE)

Convert the following schematic to (a) SPICE, (b) truth table, (c) logic gates (d) logic expression.



```
.SUBCKT GATE1X 1 2 3 4 5 6
* .SUBCKT GATE1X A1=1 B1=2 C1=3 D1=4 Q1=5 VDD=6
*
*Mname DRAIN GATE SOURCE SUBSTRATE MODEL WIDTH LENGTH
*      NODE  NODE  NODE   NODE        NAME  MICRONS MICRONS
*-----
MP0    10    3     6     6        PCH    W=20U   L=2U
MP2    7     1    10    6        PCH    W=20U   L=2U
MN0    7     2     8     0        NCH    W=5U    L=2U
MN1    8     1     0     0        NCH    W=5U    L=2U

MP1    10    4     6     6        PCH    W=20U   L=2U
MP3    7     2    10    6        PCH    W=20U   L=2U
MN2    7     3     9     0        NCH    W=5U    L=2U
MN3    9     4     0     0        NCH    W=5U    L=2U

MP4    5     7     6     6        PCH    W=20U   L=2U
MN4    5     7     0     0        NCH    W=6U    L=2U

.ENDS GATE1X



*MODEL NAME TYPE; 2 Micron process technology
*-----
.model NCH nmos LEVEL=1 KP=48E-6 LAMBDA=0.032
      VTO=0.88 GAMMA=0.66 PHI=0.7
.model PCH pmos LEVEL=1 KP=16E-6 LAMBDA=0.044
      VTO=-0.85 GAMMA=0.69 PHI=0.7
```

Compare this with with the CMOS AND-OR-INVERT gate Fig. 3-20 in Wakerly's book.

  
# 1b: flow model



Another way to view CMOS logic is the box flow model



flow model of a NOT Gate

 

1





0

# 1b: flow model

Convert the following schematic to (a) SPICE, (b) truth table, (c) logic gates (e) logic expression.

## Rewrite the circuit as a flow model

 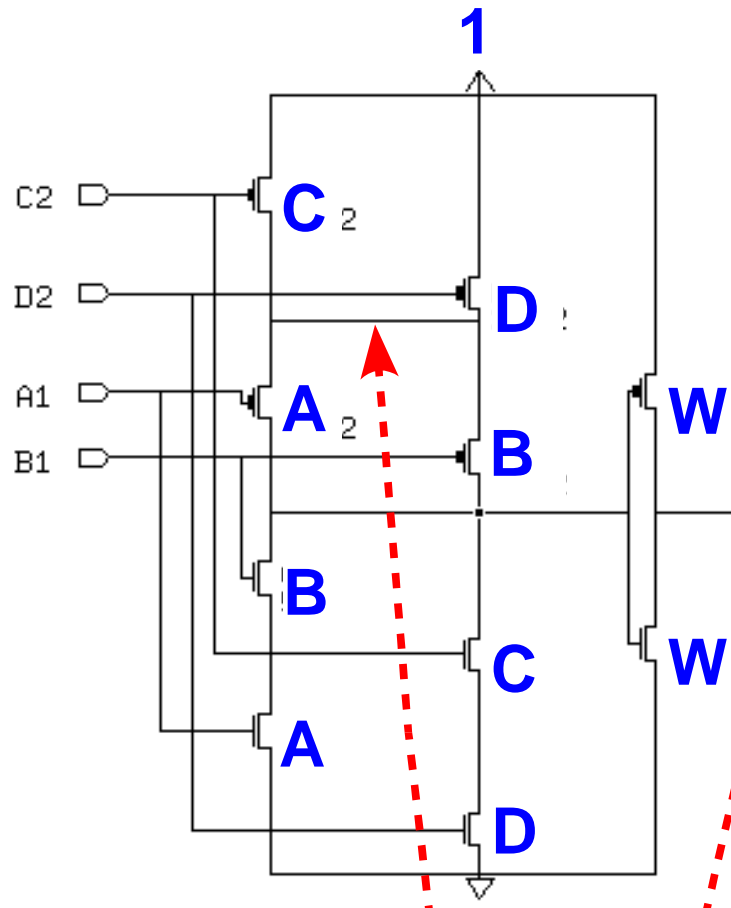

Notice these connections

# 1b: flow model

Another way to view this (where x=1 or 0=Don't Care):

$W_1$  becomes 1 when  $C=0$  &  $A=0$  otherwise Z

$\Rightarrow Ax\bar{C}x \Rightarrow 0x0x \Rightarrow 0000, 0001, 0100, 0100$

Also,  $W_1$  becomes 1 when  $D=0$  &  $A=0$  & otherwise Z

$\Rightarrow Axx\bar{D} \Rightarrow 0xx0 \Rightarrow 0000, 0010, 0100, 0110$

$W_2$  becomes 1 when  $(D=0 \text{ \& } B=0)$  OR  $(C=0 \text{ \& } B=0)$  otherwise Z

$\Rightarrow xB\bar{D} \Rightarrow x0x0 \Rightarrow 0000, 0010, 1000, 1010$

$\Rightarrow x\bar{B}\bar{C}x \Rightarrow x00x \Rightarrow 0000, 0001, 1000, 1001$


OVERLAP: notice  $W_3$  and  $W_4$  overlaps when ABCD is equal to 1111 that is ok because the result  $W_3 = 1$   $W_4 = 1$  it's when the differ, it's bad!

$W_4$  becomes 0 only when  $D=1$  &  $C=1$

$\Rightarrow xx\bar{C}D \Rightarrow xx11 \Rightarrow 0011, 0111, 1011, 1011$

$W_3$  becomes 0 only when  $A=1$  &  $B=1$

 $\Rightarrow \bar{A}Bxx \Rightarrow 11xx \Rightarrow 1100, 1101, 1110, 1111$



# 1b: Truth Table (behavior)



$W_1$  is Z otherwise is 1 when  
 $\Rightarrow AxCx \Rightarrow 0x0x \Rightarrow \underline{0000}, 0001, 0100, 0101$   
 $\Rightarrow AxxD \Rightarrow 0xx0 \Rightarrow \underline{0000}, 0010, 0100, 0110$

$W_2$  is Z otherwise is 1 when  
 $\Rightarrow xBxD \Rightarrow x0x0 \Rightarrow \underline{0000}, 0010, 1000, 1010$   
 $\Rightarrow xBCx \Rightarrow x00x \Rightarrow \underline{0000}, 0001, 1000, 1001$

$W_3$  becomes 0 when  $A=1 \ \& \ B=1$  otherwise Z  
 $\Rightarrow ABxx \Rightarrow 11xx \Rightarrow 1100, 1101, 1110, \underline{1111}$

$W_4$  becomes 0 when  $C=1 \ \& \ D=1$  otherwise Z  
 $\Rightarrow xxCD \Rightarrow xx11 \Rightarrow 0011, 0111, 1011, \underline{1111}$


$W = W_1 \text{ OR } W_2 \text{ OR } W_3 \text{ OR } W_4$   
 $Q = \text{NOT}(W) = \text{NOT}(W_1 \text{ OR } W_2 \text{ OR } W_3 \text{ OR } W_4)$

Cases of ABCD	
$W_1, W_1, W_2, W_2:$	$0x0x, 0xx0, x0x0, x00x$
$W_1, W_2:$	$0x0x, x00x$
$W_1, W_2:$	$0xx0, x0x0$
$W_4:$	$xx11$
$W_1, W_1:$	$0x0x, 0xx0$
$W_2:$	$0x0x$
$W_1:$	$0xx0$
$W_4:$	$xx11$
$W_2:$	$x0x0, x00x$
$W_2:$	$x00x$
$W_2:$	$x0x0$
$W_4:$	$xx11$
$W_3:$	$11xx$
$W_3:$	$11xx$
$W_3:$	$11xx$
$W_3, W_4:$	$xx11, 11xx$

A	B	C	D	$W_1$	$W_2$	$W_3$	$W_4$	W	Q
0	0	0	0	1	1	Z	Z	1	0
0	0	0	1	1	1	Z	Z	1	0
0	0	1	0	1	1	Z	Z	1	0
0	0	1	1	Z	Z	Z	0	0	1
0	1	0	0	1	Z	Z	Z	1	0
0	1	0	1	1	Z	Z	Z	1	0
0	1	1	1	Z	Z	Z	0	0	1
1	0	0	0	Z	1	Z	Z	1	0
1	0	0	1	Z	1	Z	Z	1	0
1	0	1	0	Z	1	Z	Z	1	0
1	0	1	1	Z	Z	Z	0	0	1
1	1	0	0	Z	Z	0	Z	0	1
1	1	0	1	Z	Z	0	Z	0	1
1	1	1	0	Z	Z	0	Z	0	1
1	1	1	1	Z	Z	0	0	0	1

# 1c: Logic Gate Level

A	B	C	D	Q	SOP
0	0	0	0	0	
0	0	0	1	0	
0	0	1	0	0	
0	0	1	1	1	$\bar{A} \bar{B} C D$
0	1	0	0	0	
0	1	0	1	0	
0	1	0	1	0	
0	1	1	1	1	$\bar{A} B C D$
1	0	0	0	0	
1	0	0	1	0	
1	0	1	0	0	
1	0	1	1	1	$A \bar{B} C D$
1	1	0	0	1	$A B \bar{C} \bar{D}$
1	1	0	1	1	$A B \bar{C} D$
1	1	1	0	1	$A B C \bar{D}$
1	1	1	1	1	$A B C D$

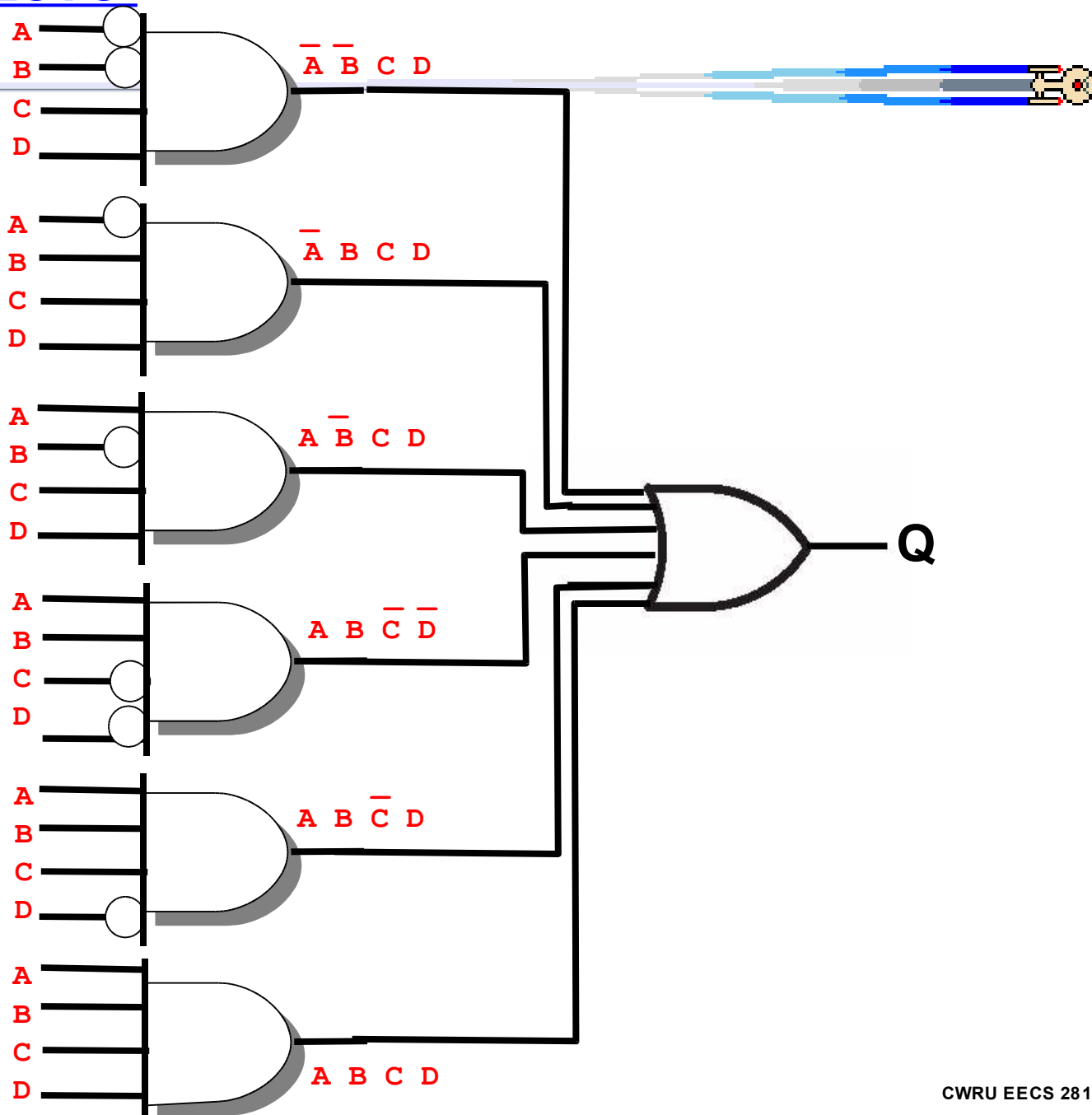

# 1d: Logic Expression




A	B	C	D	Q	SOP
0	0	0	0	0	
0	0	0	1	0	
0	0	1	0	0	
0	0	1	1	1	$\bar{A} \bar{B} C D$
0	1	0	0	0	
0	1	0	1	0	
0	1	0	1	0	
0	1	1	1	1	$\bar{A} B C D$
1	0	0	0	0	
1	0	0	1	0	
1	0	1	0	0	
1	0	1	1	1	$A \bar{B} C D$
1	1	0	0	1	$A B \bar{C} \bar{D}$
1	1	0	1	1	$A B \bar{C} D$
1	1	1	0	1	$A B C \bar{D}$
1	1	1	1	1	$A B C D$

$$Q = (\bar{A} \& \bar{B} \& C \& D) \\ | (\bar{A} \& B \& C \& D) \\ | (A \& \bar{B} \& C \& D) \\ | (A \& B \& \bar{C} \& \bar{D}) \\ | (A \& B \& \bar{C} \& D) \\ | (A \& B \& C \& \bar{D}) \\ | (A \& B \& C \& D);$$

## 2a: Logic Expression

Re-write the following schematic as two logic expressions, sum=?  
And cout=? (b) as VHDL (c) and convert schematic using only NORs.

 **sum = cin ^ (a ^ b) = cin XOR (a XOR b);**




**VHDL: cout = ( ((a AND b) OR (a AND cin)) OR (b AND cin) );**

**C/C++: cout = ( ((a & b) | (a & cin)) | (b & cin) );**


 
## 2b: VHDL

Re-write the following schematic as two logic expressions, sum=?  
And cout=? (b) as VHDL (c) and convert schematic using only NORs.



```
ENTITY P2 IS  
  PORT ( a, b, cin: IN std_logic;  
         Sum, Cout: OUT std_logic  
        );  
END P2;
```

```
ARCHITECTURE P2A OF P2 IS
```

```
BEGIN
```

```
  sum <= cin XOR (a XOR b);
```

```
  cout <= ((a AND b) OR (a AND cin))
```


```
           OR (b AND cin);
```

```
END P2A;
```

 
# 2c: AND-to-NOR, NOT-to-NOR, OR-to-NOR Transforms

Re-write the following schematic as two logic expressions, sum=?


And cout=? (b) as VHDL (c) and convert schematic using only NORs.




**DeMorgans Law:**

 

**X = NOT(NOT x):**

 

**NOT(X) = NOT(X OR X) = X NOR X;**

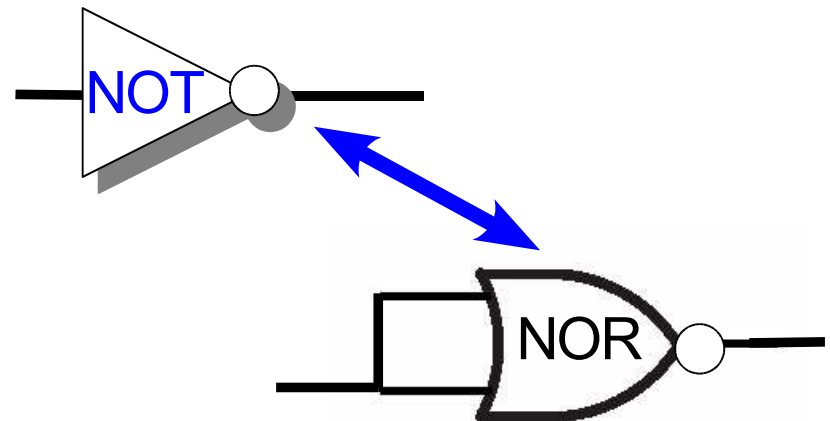

# 2c: XOR Transform



— Truth Table: behavior

x	y	$f_{xor}$	XOR
0	0	0	
0	1	1	$\sim x \ \& \ y$
1	0	1	$x \ \& \ \sim y$
1	1	0	

SOP

Gate Level

DeMorgan's Law

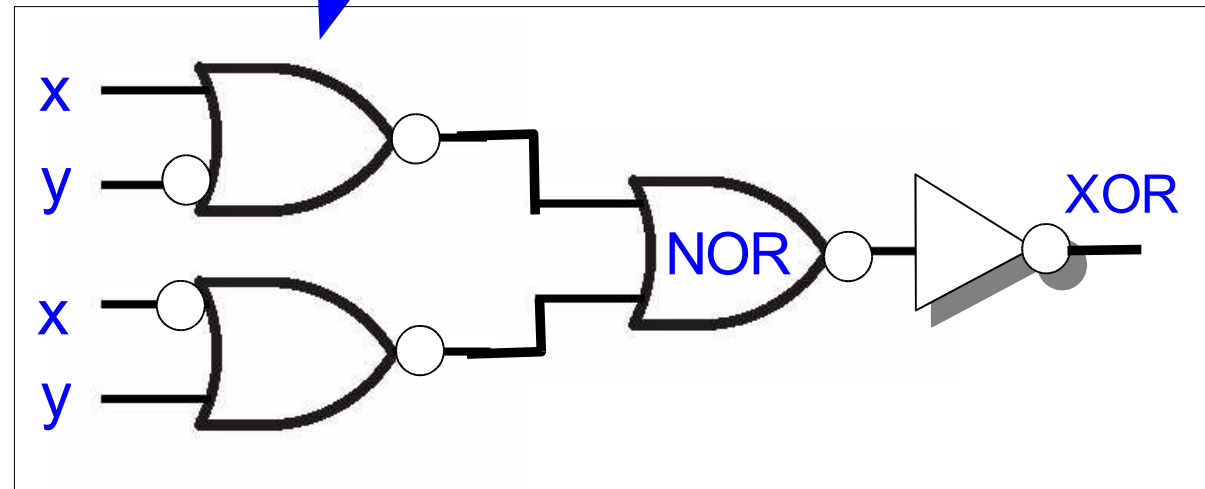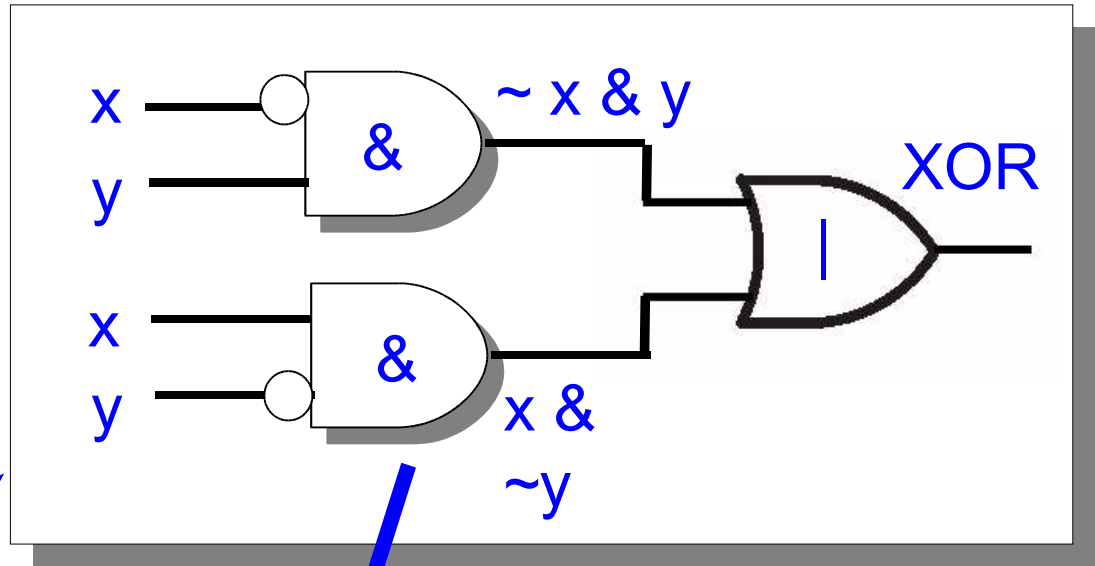

$$XOR = (\sim x \ \& \ y) \ | \ (x \ \& \ \sim y)$$

# 2c: XOR Transform



Replace every XOR with the following structural circuit:

